

Assignment

12.8 - 6

EE23BTECH11220 - R.V.S.S Varun

QUESTION

A charged $30\ \mu\text{F}$ capacitor is connected to a $27\ \text{mH}$ inductor. Suppose the initial charge on the capacitor is 6mC . What is the total energy stored in the circuit initially? What is the total energy at later time?

SOLUTION